

Problem-1

- Source code

```
//module declaration with inputs and outputs
module p1(Y,present,clock,reset,input_bit);

//Conventionally output is declared first, then input.
    output Y;
    input clock, reset,input_bit;
    output [2:0] present;
    reg [2:0] next;
    reg[2:0] present;

    parameter [2:0] S0=3'b000;
    parameter [2:0] S1=3'b001;
    parameter [2:0] S2=3'b010;
    parameter [2:0] S3=3'b011;
    parameter [2:0] S4=3'b100;

    initial
    begin
        present = 3'b000;
        next = 3'b000;
    end

    always @(posedge clock)
// sequential logic
    begin
        if (reset) present <= S0;
        else present <= next;
```

```

        end

// combinational logic
        always @(present or input_bit) // combinational logic
        begin
            case(present)
                S0: if (reset) next = S0;
                    else if(input_bit) next = S1;
                    else next = S0;

                S1: if (reset) next = S0;
                    else if(input_bit) next = S2;
                    else next = S0;

                S2: if (reset) next = S0;
                    else if(input_bit) next = S2;
                    else next = S3;

                S3: if (reset) next = S0;
                    else if(input_bit) next = S4;
                    else next = S0;

                S4: if (reset) next = S0;
                    else if(input_bit) next = S2;
                    else next = S0;

            endcase

        end

// output logic described using continuous assignment
        assign Y = (present == S4);
    endmodule

```

- Test bench for p1.v

```

module tb_p1();
    reg clock, reset,input_bit;

    wire Y;

```

```

wire[2:0] present;

integer i;

p1 UUT(Y,present,clock,reset,input_bit);

reg[20:1] Sequence = 20'b11101101001001101101;

initial reset = 1'b1;

always #10 clock = ~clock;

initial
    begin
        clock = 1'b1;
        reset = 1'b0;
        for (i=20;i>0;i=i-1)
            begin
                input_bit = Sequence[i]; #20
                $monitor("Sequence Bit = %b | Output = %b | reset = %b\n time=",
input_bit, Y, reset, $time);
            end
        end
    end
endmodule

```

- Transcript


```


# Sequence Bit = 1 | Output = 0 | reset = 0
# time=          20
# Sequence Bit = 1 | Output = 0 | reset = 0
# time=          40
# Sequence Bit = 0 | Output = 0 | reset = 0
# time=          60
# Sequence Bit = 1 | Output = 0 | reset = 0
# time=          80
# Sequence Bit = 1 | Output = 1 | reset = 0
# time=         100
# Sequence Bit = 0 | Output = 0 | reset = 0

```

```
# time=          120
# Sequence Bit = 1 | Output = 0 | reset = 0
# time=          140
# Sequence Bit = 0 | Output = 1 | reset = 0
# time=          160
# Sequence Bit = 0 | Output = 0 | reset = 0
# time=          180
# Sequence Bit = 1 | Output = 0 | reset = 0
# time=          200
# Sequence Bit = 0 | Output = 0 | reset = 0
# time=          220
# Sequence Bit = 0 | Output = 0 | reset = 0
# time=          240
# Sequence Bit = 1 | Output = 0 | reset = 0
# time=          260
# Sequence Bit = 1 | Output = 0 | reset = 0
# time=          280
# Sequence Bit = 0 | Output = 0 | reset = 0
# time=          300
# Sequence Bit = 1 | Output = 0 | reset = 0
# time=          320
# Sequence Bit = 1 | Output = 1 | reset = 0
# time=          340
# Sequence Bit = 0 | Output = 0 | reset = 0
# time=          360
# Sequence Bit = 1 | Output = 0 | reset = 0
# time=          380
# Sequence Bit = 1 | Output = 1 | reset = 0
# time=          400
# Sequence Bit = 1 | Output = 0 | reset = 0
# time=          420
```


File Edit View Compile Simulate Add Wave Tools Layout Bookmarks Window Help

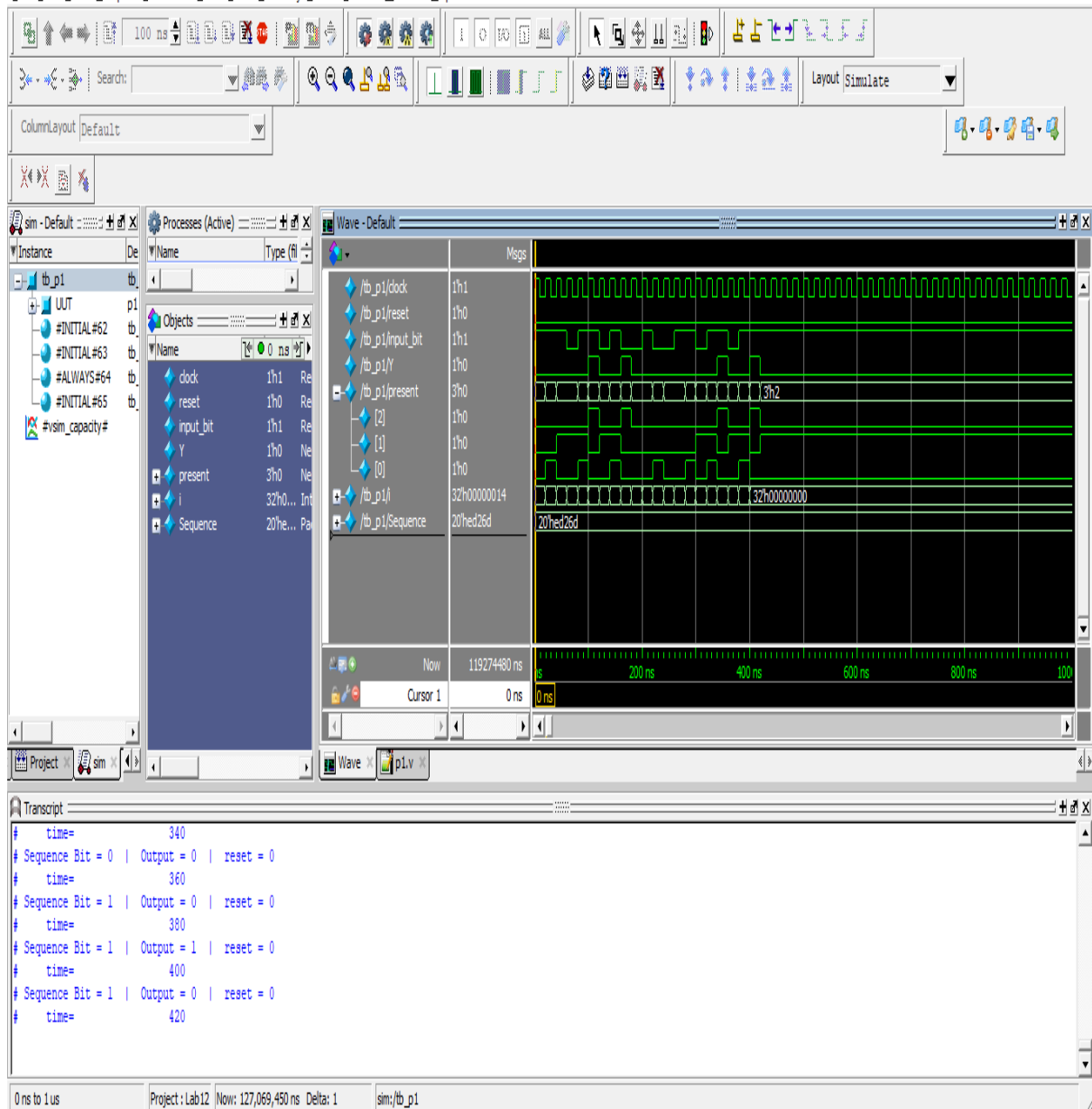

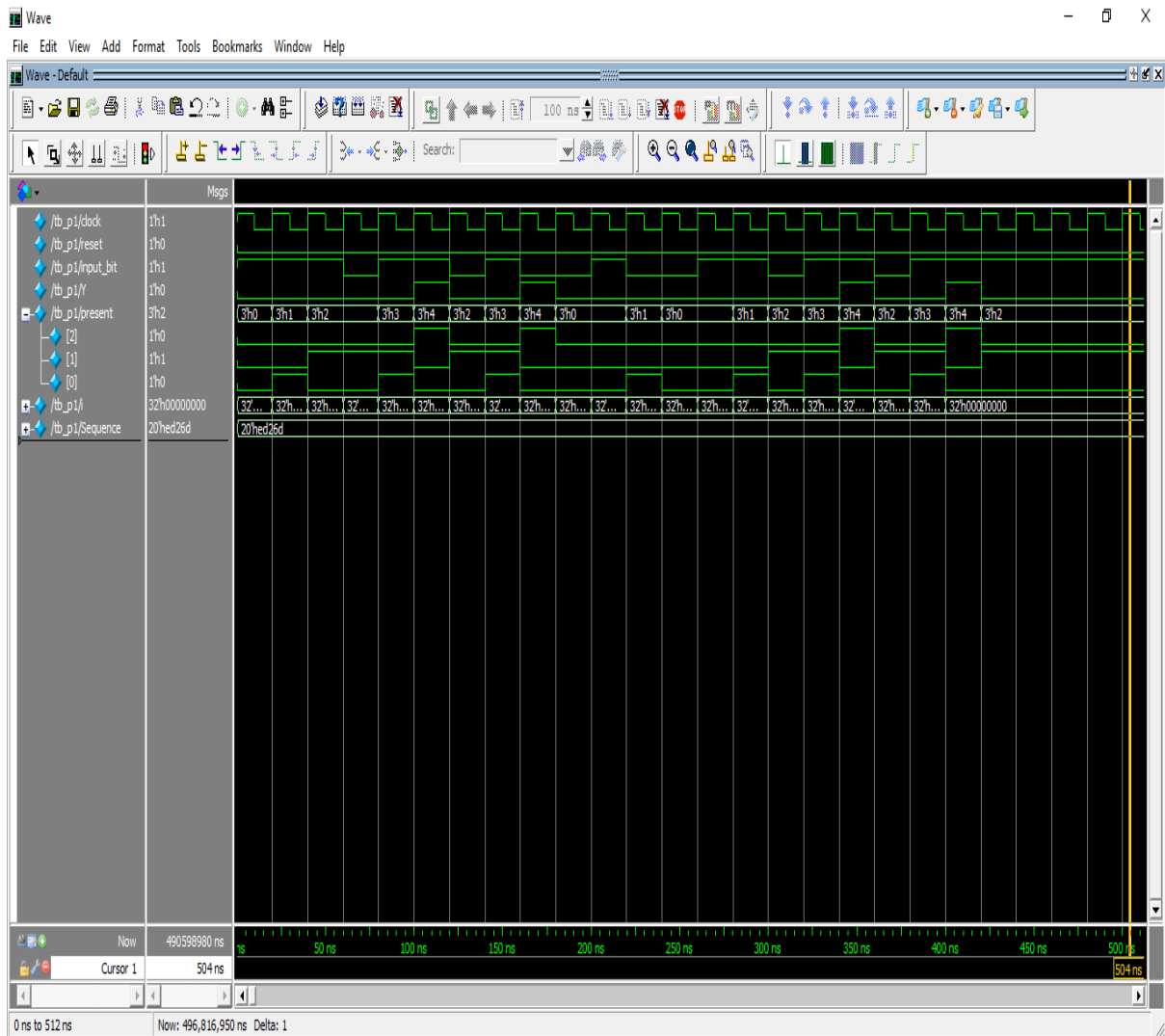

Problem 2

- Source Code

```
module p2(Q,upper,reset,clk); //counter module with inputs and outputs
```

```
//conventionally outputs are declared first, then input.
```

```
output reg [3:0]Q;
```

```
output upper;
```

```
input reset;
```

```
input clk;
```

```

always@(posedge clk)
begin
    if(reset) //reset
        Q = 4'b0000;
    else
        Q = Q + 4'b0001; //increment by 1
    end
    assign upper = Q[3];
endmodule

```

- Test Bench

```

module tb_p2(); //Test Bench
    reg clk, reset;
    wire upper;
    wire [3:0]Q;
    p2 UUT(Q, upper, reset, clk);

    initial begin //clock definition
        clk = 0;
        forever #5 clk = ~clk;
    end

    initial begin //simulation
        $monitor("COUNT = %b", Q, " | UPPER = %b", upper);
        reset = 1;
        #20;
        reset = 0;

        //stop after 500 time units
        #500 $finish;
    end
endmodule

```


- Transcript


```
# COUNT = xxxx | UPPER = x
# COUNT = 0000 | UPPER = 0
# COUNT = 0001 | UPPER = 0
# COUNT = 0010 | UPPER = 0
# COUNT = 0011 | UPPER = 0
# COUNT = 0100 | UPPER = 0
# COUNT = 0101 | UPPER = 0
# COUNT = 0110 | UPPER = 0
# COUNT = 0111 | UPPER = 0
# COUNT = 1000 | UPPER = 1
# COUNT = 1001 | UPPER = 1
# COUNT = 1010 | UPPER = 1
# COUNT = 1011 | UPPER = 1
# COUNT = 1100 | UPPER = 1
# COUNT = 1101 | UPPER = 1
# COUNT = 1110 | UPPER = 1
# COUNT = 1111 | UPPER = 1
# COUNT = 0000 | UPPER = 0
# COUNT = 0001 | UPPER = 0
# COUNT = 0010 | UPPER = 0
# COUNT = 0011 | UPPER = 0
# COUNT = 0100 | UPPER = 0
# COUNT = 0101 | UPPER = 0
# COUNT = 0110 | UPPER = 0
# COUNT = 0111 | UPPER = 0
# COUNT = 1000 | UPPER = 1
# COUNT = 1001 | UPPER = 1
# COUNT = 1010 | UPPER = 1
# COUNT = 1011 | UPPER = 1
# COUNT = 1100 | UPPER = 1
```


COUNT = 1101 | UPPER = 1
COUNT = 1110 | UPPER = 1
COUNT = 1111 | UPPER = 1
COUNT = 0000 | UPPER = 0
COUNT = 0001 | UPPER = 0
COUNT = 0010 | UPPER = 0
COUNT = 0011 | UPPER = 0
COUNT = 0100 | UPPER = 0
COUNT = 0101 | UPPER = 0
COUNT = 0110 | UPPER = 0
COUNT = 0111 | UPPER = 0
COUNT = 1000 | UPPER = 1
COUNT = 1001 | UPPER = 1
COUNT = 1010 | UPPER = 1
COUNT = 1011 | UPPER = 1
COUNT = 1100 | UPPER = 1
COUNT = 1101 | UPPER = 1
COUNT = 1110 | UPPER = 1
COUNT = 1111 | UPPER = 1
COUNT = 0000 | UPPER = 0
COUNT = 0001 | UPPER = 0
COUNT = 0010 | UPPER = 0

Wave

- □ X

 File Edit View Add Format Tools Bookmarks Window Help



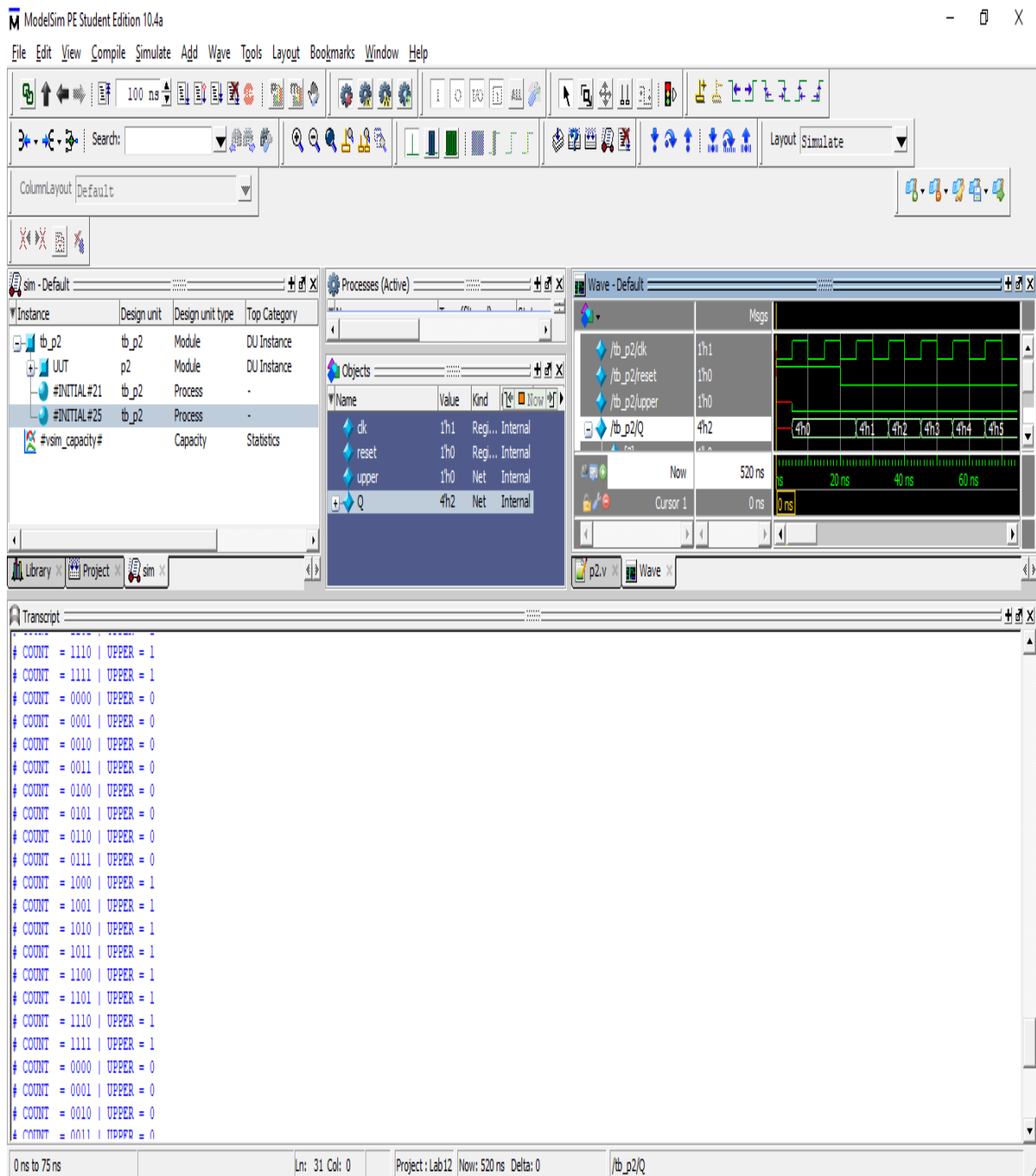

Problem-3

- Source code

```
module p3(open,clk,reset, c0,c1);
```

```
output[2:0] open;
```

```
input clk, reset;
```

```

input c0,c1;
reg [2:0] Next;
reg[2:0] state;
parameter [2:0] S0= 3'b000;
parameter [2:0] S1= 3'b001;
parameter [2:0] S2 = 3'b010;
parameter [2:0] S3=3'b011;
parameter [2:0] S4=3'b100;
parameter [2:0] S5=3'b101;
parameter [2:0] S6=3'b110;
parameter [2:0] S7=3'b111;

always @(posedge clk) // sequential
begin
if (reset) state <= S0;
else state <= Next;
end

always @(state,c0,c1) // combinational
begin
case(state)
S0: if (!c0 && c1)
        Next = S1;
    else if (c0 && !c1)
        Next = S7;
    else if(c0 && c1)
        Next = S2;
S1: if (!c0 && c1)
        Next = S2;
    else if (c0 && !c1)
        Next = S0;

```

```
else if(c0 && c1)
    Next = S3;
```

```
S2: if (!c0 && c1)
    Next = S3;
else if (c0 && !c1)
    Next = S1;
else if(c0 && c1)
    Next = S4;
```

```
S3: if (!c0 && c1)
    Next = S4;
else if (c0 && !c1)
    Next = S2;
else if(c0 && c1)
    Next = S5;
```

```
S4:if (!c0 && c1)
    Next = S5;
else if (c0 && !c1)
    Next = S3;
else if(c0 && c1)
    Next = S6;
```

```
S5:if (!c0 && c1)
    Next = S6;
else if (c0 && !c1)
    Next = S4;
else if(c0 && c1)
    Next = S7;
```

```
S6:if (!c0 && c1)
```

```
    Next = S7;
```

```
    else if (c0 && !c1)
```

```
        Next = S5;
```

```
    else if(c0 && c1)
```

```
        Next = S0;
```

```
S7:if (!c0 && c1)
```

```
    Next = S0;
```

```
    else if (c0 && !c1)
```

```
        Next = S6;
```

```
    else if(c0 && c1)
```

```
        Next = S1;
```

```
    endcase end
```

```
// output logic described using continuous assignment
```

```
assign open = Next;
```

```
endmodule
```

- Test Bench

```
module tb_p3();
```

```
    reg reset;
```

```
    wire[2:0] open;
```

```
    reg clk=0;
```

```
reg c0,c1;
```

```
p3 uut (open,clk,reset, c0,c1);
```

```
always #5 clk = ~clk;
```

```
initial
```

```
begin
```

```
reset=1'b1; #10;
```

```
reset=1'b0; c0=1'b0;c1=1'b1;#10;
```

```
reset=1'b0; c0=1'b1;c1=1'b0;#10;
```

```
reset=1'b0; c0=1'b1;c1=1'b1;#10;
```

```
reset=1'b0; c0=1'b0;c1=1'b0;#10;
```

```
reset=1'b1; #10;
```


```
reset=1'b0; c0=1'b0;c1=1'b1;#10;
```


```
reset=1'b0; c0=1'b0;c1=1'b1;#10;
```

```
reset=1'b1; #10;
```


```
end
```

```
endmodule
```

 


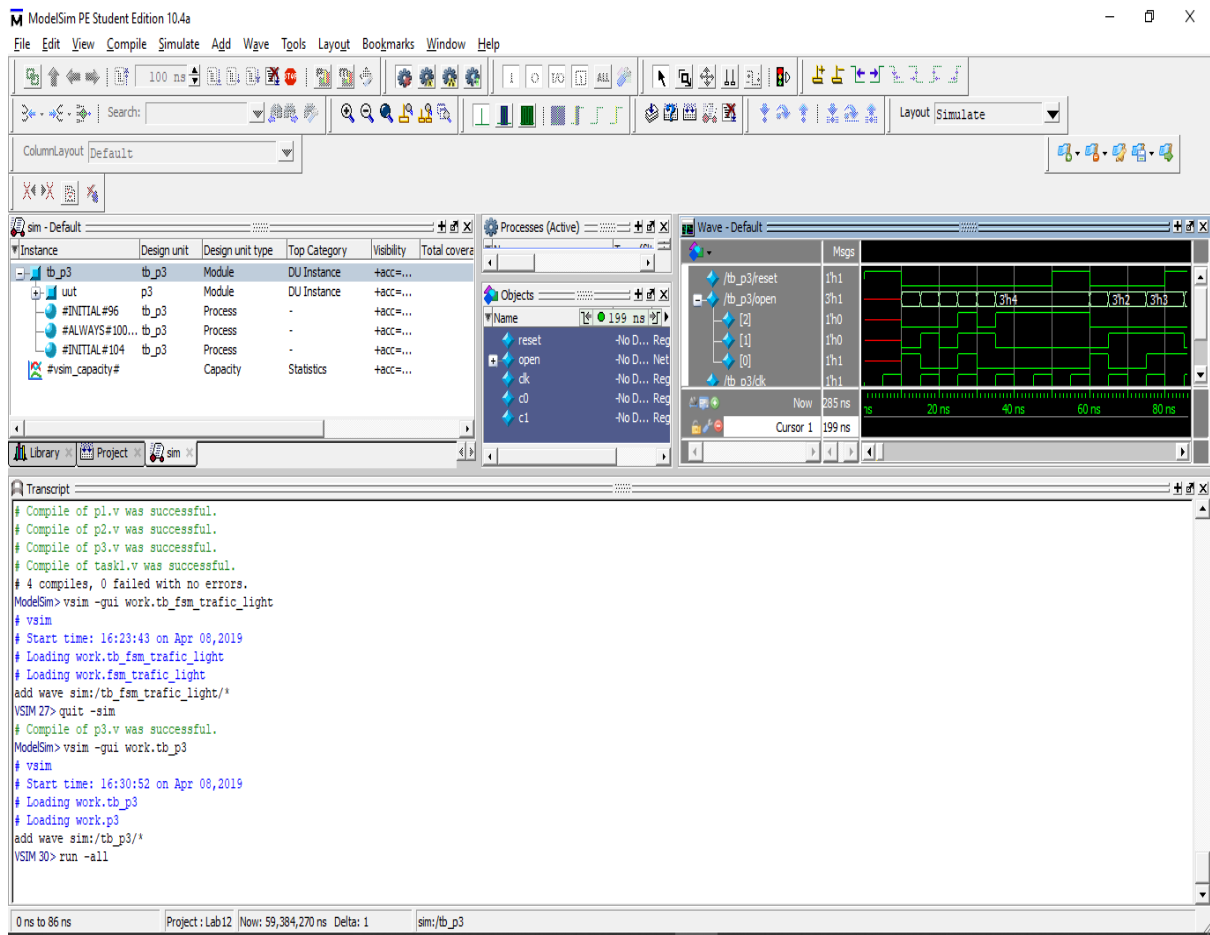


Task-1

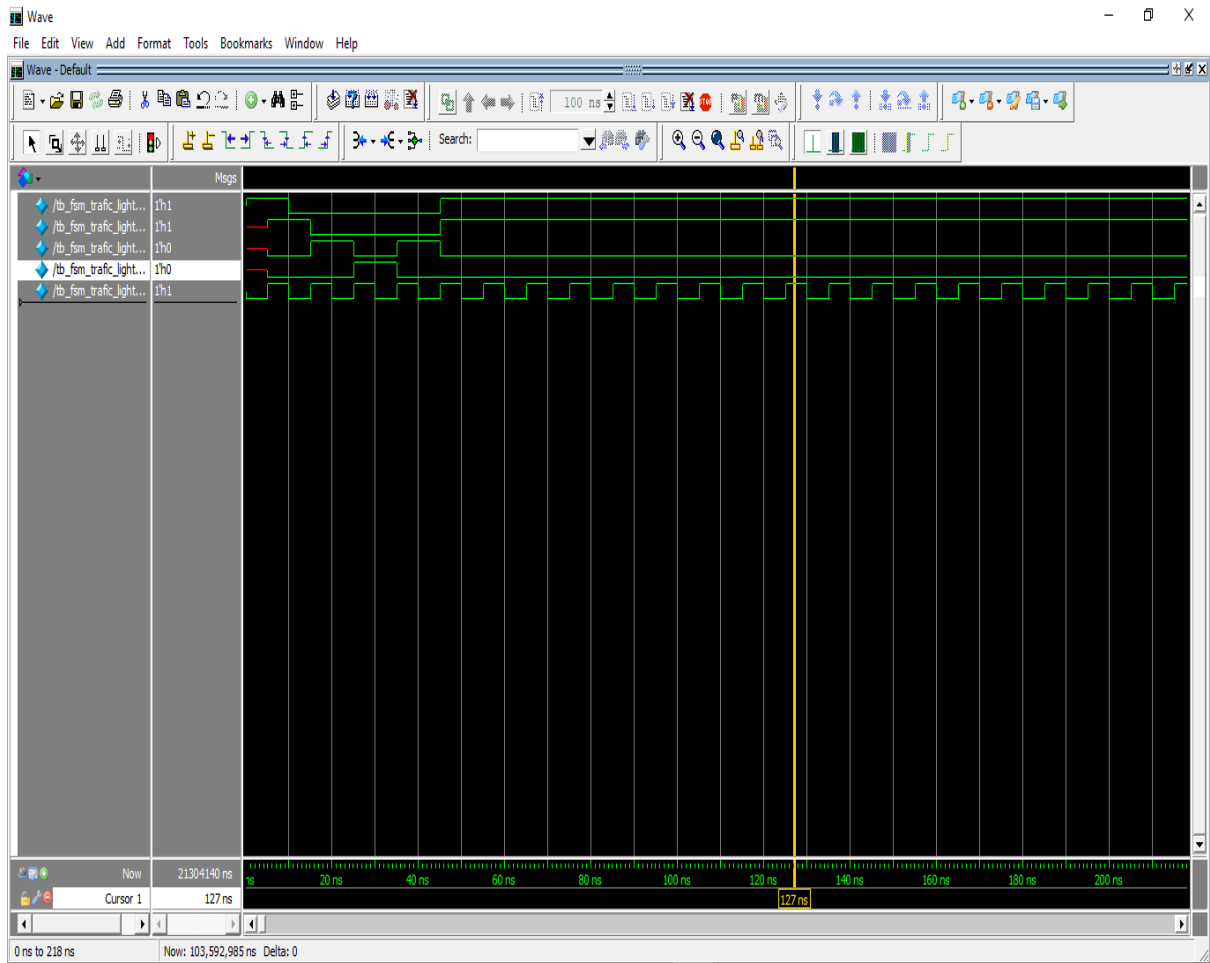

TASK-2

 

TASK-3

